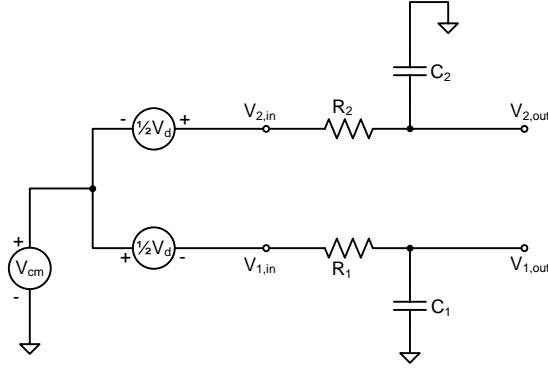


Case 1: RC filter on high and low-side



$$\frac{V_{2,out}}{V_{2,in}} = G_2(s) = \frac{1}{R_2 C_2 s + 1}$$

$$\frac{V_{1,out}}{V_{1,in}} = G_1(s) = \frac{1}{R_1 C_1 s + 1}$$

The outputs are defined as follows: $V_{diff,out} \equiv V_{2,out} - V_{1,out}$ $V_{cm,out} \equiv \frac{V_{2,out} + V_{1,out}}{2} = \text{avg}(V_{2,out}, V_{1,out})$

The relevant TF's are:

$$\frac{V_{diff,out}}{V_{diff,in}} = \frac{G_2 + G_1}{2}$$

$$\frac{V_{cm,out}}{V_{diff,in}} = \frac{G_2 - G_1}{4}$$

$$\frac{V_{diff,out}}{V_{cm,in}} = G_2 - G_1$$

$$\frac{V_{cm,out}}{V_{cm,in}} = \frac{G_2 + G_1}{2}$$

Let's define: $\tau_1 \equiv R_1 C_1$ $\tau_2 \equiv R_2 C_2$

$$\frac{V_{diff,out}}{V_{diff,in}} = \frac{G_2 + G_1}{2} = \frac{1}{2} \left(\frac{1}{\tau_2 s + 1} + \frac{1}{\tau_1 s + 1} \right) = \frac{1}{2} \frac{(\tau_1 s + 1) + (\tau_2 s + 1)}{(\tau_2 s + 1)(\tau_1 s + 1)} = \frac{1}{2} \frac{(\tau_1 + \tau_2) s + 2}{(\tau_2 s + 1)(\tau_1 s + 1)}$$

And now define: $\hat{\tau} \equiv \frac{\tau_1 + \tau_2}{2} = \text{avg}(\tau_1, \tau_2)$

This yields:



$$\boxed{\frac{V_{diff,out}}{V_{diff,in}} = \frac{\hat{\tau} s + 1}{(\tau_2 s + 1)(\tau_1 s + 1)}}$$

Note that the transfer function from CM input to CM output is the same.


$$\boxed{\frac{V_{diff,out}}{V_{cm,in}} = G_2 - G_1 = \frac{1}{\tau_2 s + 1} - \frac{1}{\tau_1 s + 1} = \frac{(\tau_1 s + 1) - (\tau_2 s + 1)}{(\tau_2 s + 1)(\tau_1 s + 1)} = (\tau_1 - \tau_2) \frac{s}{(\tau_2 s + 1)(\tau_1 s + 1)}}$$

$$\boxed{\frac{V_{cm,out}}{V_{diff,in}} = \frac{G_2 - G_1}{4} = \left(\frac{\tau_1 - \tau_2}{4} \right) \frac{s}{(\tau_2 s + 1)(\tau_1 s + 1)}}$$

Let's look at the qualitative Bode Plot's.

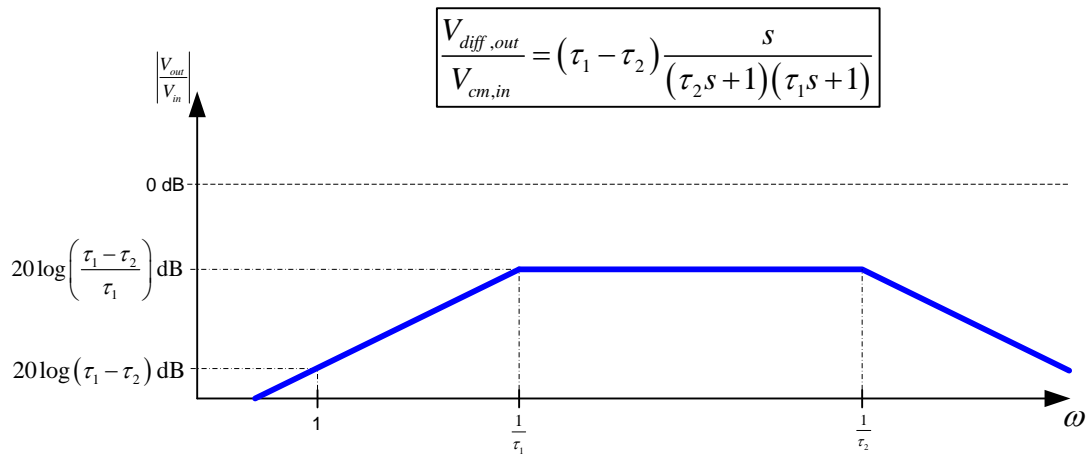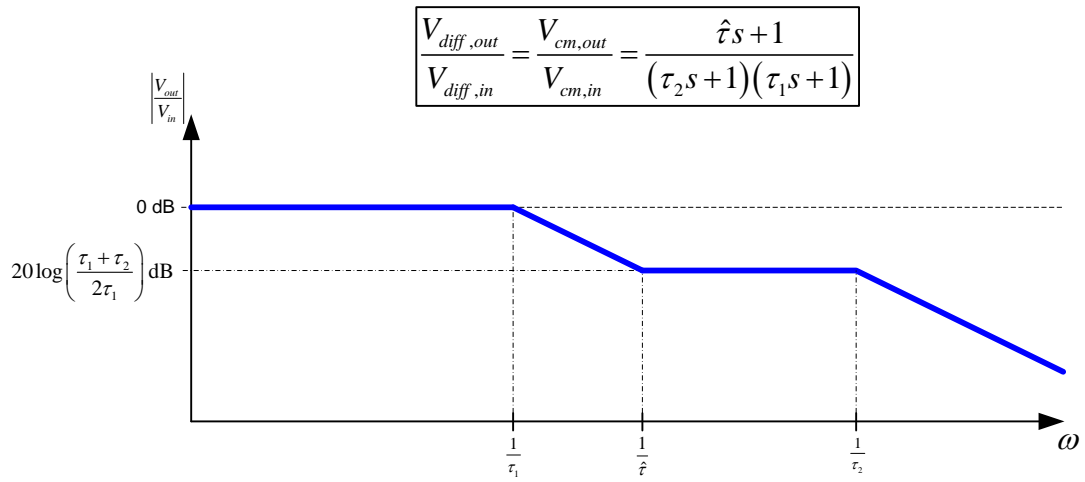

Case 2: Case 1 plus C_3 across output

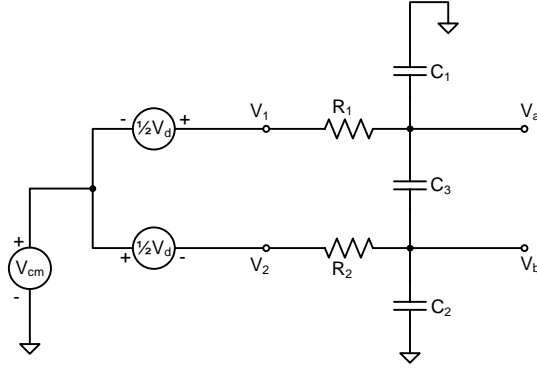

$$\frac{V_1 - V_a}{R_1} = C_1 V_a' + C_3 (V_a' - V_b')$$

$$\frac{V_2 - V_b}{R_2} = C_2 V_b' + C_3 (V_b' - V_a')$$

$$V_1 = [R_1 (C_1 + C_3) s + 1] V_a - R_1 C_3 s V_b$$

$$V_2 = [R_2 (C_2 + C_3) s + 1] V_b - R_2 C_3 s V_a$$

$$\begin{bmatrix} R_1 (C_1 + C_3) s + 1 & -R_1 C_3 s \\ -R_2 C_3 s & R_2 (C_2 + C_3) s + 1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

In state-space form, it is...

$$\dot{\mathbf{x}} = \mathbf{A}\mathbf{x} + \mathbf{B}\mathbf{u}$$

$$\mathbf{y} = \mathbf{C}\mathbf{x} + \mathbf{D}\mathbf{u}$$

$$\mathbf{A} = \begin{bmatrix} -\frac{C_2 + C_3}{R_1 C_{eq}} & -\frac{C_3}{R_2 C_{eq}} \\ -\frac{C_3}{R_1 C_{eq}} & -\frac{C_1 + C_3}{R_2 C_{eq}} \end{bmatrix} \quad \mathbf{B} = \begin{bmatrix} \frac{1}{C_{eq}} \left(\frac{C_2 + C_3}{R_1} + \frac{C_3}{R_2} \right) & \frac{1}{C_{eq}} \left(\frac{C_2 + C_3}{2R_1} - \frac{C_3}{2R_2} \right) \\ \frac{1}{C_{eq}} \left(\frac{C_1 + C_3}{R_2} + \frac{C_3}{R_1} \right) & \frac{1}{C_{eq}} \left(\frac{C_3}{2R_1} - \frac{C_1 + C_3}{2R_2} \right) \end{bmatrix}$$


$$\mathbf{C} = \begin{bmatrix} \frac{1}{2} & \frac{1}{2} \\ 1 & -1 \end{bmatrix} \quad \mathbf{D} = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}$$

Where $C_{eq} = C_1 C_2 + C_1 C_3 + C_2 C_3$

Where the inputs, states, and outputs are:

$$\mathbf{u} = \begin{bmatrix} V_{cm,in} \\ V_{diff,in} \end{bmatrix} \quad \mathbf{x} = \begin{bmatrix} V_a \\ V_b \end{bmatrix} \quad \mathbf{y} = \begin{bmatrix} V_{cm,out} \\ V_{diff,out} \end{bmatrix}$$

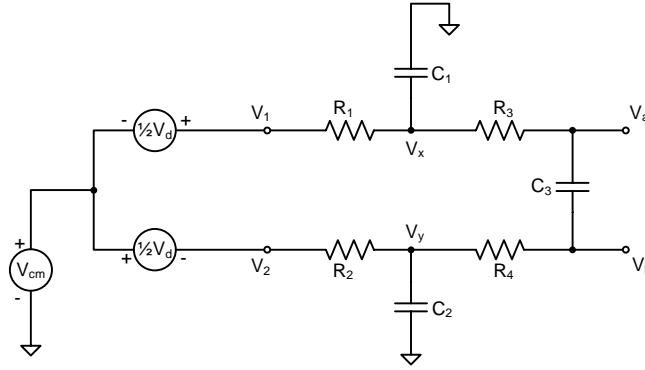Case 3: Case 1 followed by a differential low-pass



$$\text{KCL at node } V_x: \frac{V_1 - V_x}{R_1} = C_1 V'_x + \frac{V_x - V_a}{R_3} \quad \rightarrow \quad V'_x = -\left(\frac{1}{R_1 C_1} + \frac{1}{R_3 C_1}\right) V_x + \frac{1}{R_1 C_1} V_1 + \frac{1}{R_3 C_1} V_a$$

$$\text{KCL at node } V_y: \frac{V_2 - V_y}{R_2} = C_2 V'_y + \frac{V_y - V_b}{R_4} \quad \rightarrow \quad V'_y = -\left(\frac{1}{R_2 C_2} + \frac{1}{R_4 C_2}\right) V_y + \frac{1}{R_2 C_2} V_2 + \frac{1}{R_4 C_2} V_b$$

$$\text{KCL at node } V_a: \frac{V_x - V_a}{R_3} = C_3 (V'_a - V'_b) = C_3 V'_{ab} \quad \rightarrow \quad V'_{ab} = \frac{1}{R_3 C_3} V_x - \frac{1}{R_3 C_3} V_a$$

$$\text{KVL around diff. filter: } V_x - V_y = (R_3 + R_4) i + V_{ab}$$

$$\text{Substitute in: } V_1 = V_{cm} + \frac{1}{2} V_{diff} \quad \text{and} \quad V_2 = V_{cm} - \frac{1}{2} V_{diff}$$

$$\text{Substitute in: } V_a = \frac{R_4}{R_3 + R_4} V_x + \frac{R_3}{R_3 + R_4} V_y + \frac{R_3}{R_3 + R_4} V_{ab} \quad \text{and} \quad V_b = \frac{R_4}{R_3 + R_4} V_x + \frac{R_3}{R_3 + R_4} V_y - \frac{R_4}{R_3 + R_4} V_{ab}$$

$$\begin{aligned} \text{In state-space form, it becomes...} \quad & \dot{\mathbf{x}} = \mathbf{Ax} + \mathbf{Bu} \\ & \mathbf{y} = \mathbf{Cx} + \mathbf{Du} \end{aligned}$$

$$\mathbf{A} = \begin{bmatrix} -\frac{1}{C_1} \left[\frac{1}{(R_3 + R_4)} + \frac{1}{R_1} \right] & \frac{1}{C_1 (R_3 + R_4)} & \frac{1}{C_1 (R_3 + R_4)} \\ \frac{1}{C_2 (R_3 + R_4)} & -\frac{1}{C_2} \left[\frac{1}{(R_3 + R_4)} + \frac{1}{R_2} \right] & -\frac{1}{C_2 (R_3 + R_4)} \\ \frac{1}{C_3 (R_3 + R_4)} & -\frac{1}{C_3 (R_3 + R_4)} & -\frac{1}{C_3 (R_3 + R_4)} \end{bmatrix} \quad \mathbf{B} = \begin{bmatrix} \frac{1}{R_1 C_1} & \frac{1}{2R_1 C_1} \\ \frac{1}{R_2 C_2} & -\frac{1}{2R_2 C_2} \\ 0 & 0 \end{bmatrix}$$

$$\mathbf{C} = \begin{bmatrix} \frac{R_4}{R_3 + R_4} & \frac{R_3}{R_3 + R_4} & \frac{R_3 - R_4}{2(R_3 + R_4)} \\ 0 & 0 & 1 \end{bmatrix} \quad \mathbf{D} = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}$$

Where the inputs, states, and outputs are:

$$\mathbf{u} = \begin{bmatrix} V_{cm,in} \\ V_{diff,in} \end{bmatrix} \quad \mathbf{x} = \begin{bmatrix} V_x \\ V_y \\ V_a - V_b \end{bmatrix} \quad \mathbf{y} = \begin{bmatrix} V_{cm,out} \\ V_{diff,out} \end{bmatrix}$$

The TF from CM input to differential output has one (1) zero (located close to zero) and three (3) poles.